
QUESTION 1(d)

Neatly draw an electrical diagram of the following sketch.

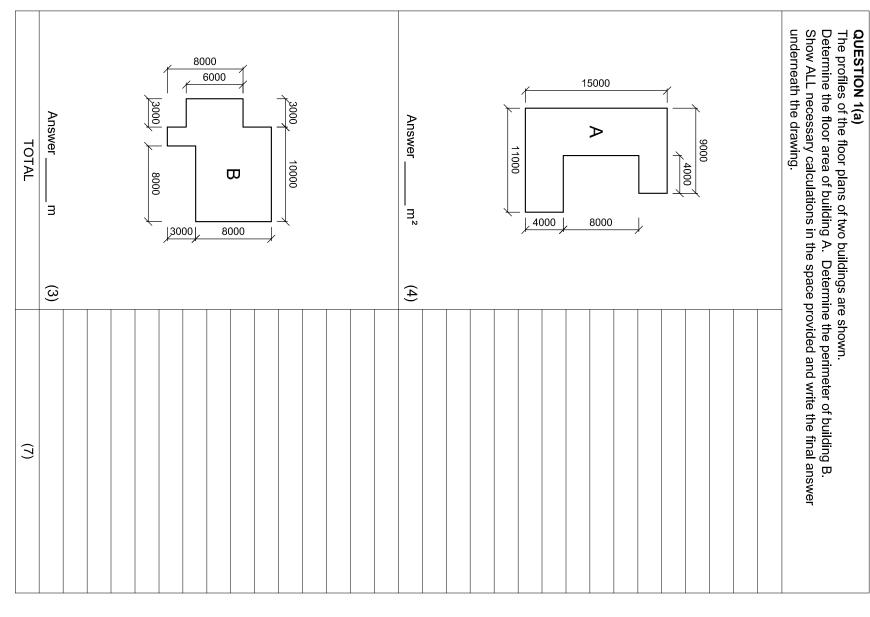

QUESTION 1: ANALYTICAL (CIVIL)



| D) Wash basin | C) Sink unit - single | B) Shower | A) Bath | Description | QUESTION 1(b) Make a neat freehand the convention given. |
|---------------|-----------------------|-----------|---------|-------------------|---|
| (2) | 0 | (2) | 0 | View in plan | QUESTION 1(b) Make a neat freehand drawing of the missing plan or elevation of the convention given. |
| | (2) | | (2) | View in elevation | plan or elevation of |



| (5) | |
|-----|--|

TOTAL

8

| 23 | 5 | З | ∞ | |
|------|----|------|---|--|
| | | | | |
| NAME | | NAME | | |
| | () | | | |

TOTAL

Question 1(d)

Question 1(b)

Question 1(a)

Question 1(c)